

Laboratory Exercise 3-4

3. Numbers and Displays

4. Adders

This is an exercise in designing combinational circuits that can perform binary-to-decimal number conversion and binary-coded-decimal (BCD) addition.

Part I 7-Segment Display of Decimal Inputs

We wish to display on the 7-segment displays *HEX3* to *HEX0* the values set by the switches *SW15-0*. Let the values denoted by *SW15-12*, *SW11-8*, *SW7-4* and *SW3-0* be displayed on *HEX3*, *HEX2*, *HEX1* and *HEX0*, respectively. Your circuit should be able to display the digits from 0 to 9, and should treat the valuations 1010 to 1111 as don't-cares.

1. Create a new project which will be used to implement the desired circuit on the Altera DE2-series board. The intent of this exercise is to manually derive the logic functions needed for the 7-segment displays. You should use only simple Verilog **assign** statements in your code and specify each logic function as a Boolean expression.
2. Write a Verilog file that provides the necessary functionality. Include this file in your project and assign the pins on the FPGA to connect to the switches and 7-segment displays, as indicated in the User Manual for the DE2-series board. The procedure for making pin assignments is described in the tutorial *Quartus II Introduction using Verilog Design*, which is available on the *DE2-Series System CD* and in the University Program section of Altera's web site.
3. Compile the project and download the compiled circuit into the FPGA chip.
4. Test the functionality of your design by toggling the switches and observing the displays.

Part II 4-bit Binary to 2-digit Decimal Converter

You are to design a circuit that converts a four-bit binary number $V = v_3v_2v_1v_0$ into its two-digit decimal equivalent $D = d_1d_0$. Table 1 shows the required output values. A partial design of this circuit is given in Figure 1. It includes a comparator that checks when the value of V is greater than 9, and uses the output of this comparator in the control of the 7-segment displays. You are to complete the design of this circuit by creating a Verilog module which includes the comparator, multiplexers, and circuit A (do not include circuit B or the 7-segment decoder at this point). Your Verilog module should have the four-bit input V , the four-bit output M and the output z . The intent of this exercise is to use simple Verilog **assign** statements to specify the required logic functions using Boolean expressions. Your Verilog code should not include any **if-else**, **case**, or similar statements.

Binary value	Decimal digits	
0000	0	0
0001	0	1
0010	0	2
...
1001	0	9
1010	1	0
1011	1	1
1100	1	2
1101	1	3
1110	1	4
1111	1	5

Table 1. Binary-to-decimal conversion values.

Perform the following steps:

1. Make a Quartus II project for your Verilog module.
2. Compile the circuit and use functional simulation to verify the correct operation of your comparator, multiplexers, and circuit A.
3. Augment your Verilog code to include circuit B in Figure 1 as well as the 7-segment decoder. Change the inputs and outputs of your code to use switches SW_{3-0} on the DE2-series board to represent the binary number V , and the displays $HEX1$ and $HEX0$ to show the values of decimal digits d_1 and d_0 . Make sure to include in your project the required pin assignments for the DE2-series board.
4. Recompile the project, and then download the circuit into the FPGA chip.
5. Test your circuit by trying all possible values of V and observing the output displays.

 


Figure 1: Partial design of the binary-to-decimal conversion circuit.

Part III 4-bit Ripple Carry Adder

Figure 2a shows a circuit for a *full adder*, which has the inputs a , b , and c_i , and produces the outputs s and c_o . Parts b and c of the figure show a circuit symbol and truth table for the full adder, which produces the two-bit binary sum $c_o s = a + b + c_i$. Figure 2d shows how four instances of this full adder module can be used to design a circuit that adds two four-bit numbers. This type of circuit is usually called a *ripple-carry* adder, because of the way that the carry signals are passed from one full adder to the next. Write Verilog code that implements this circuit, as described below.

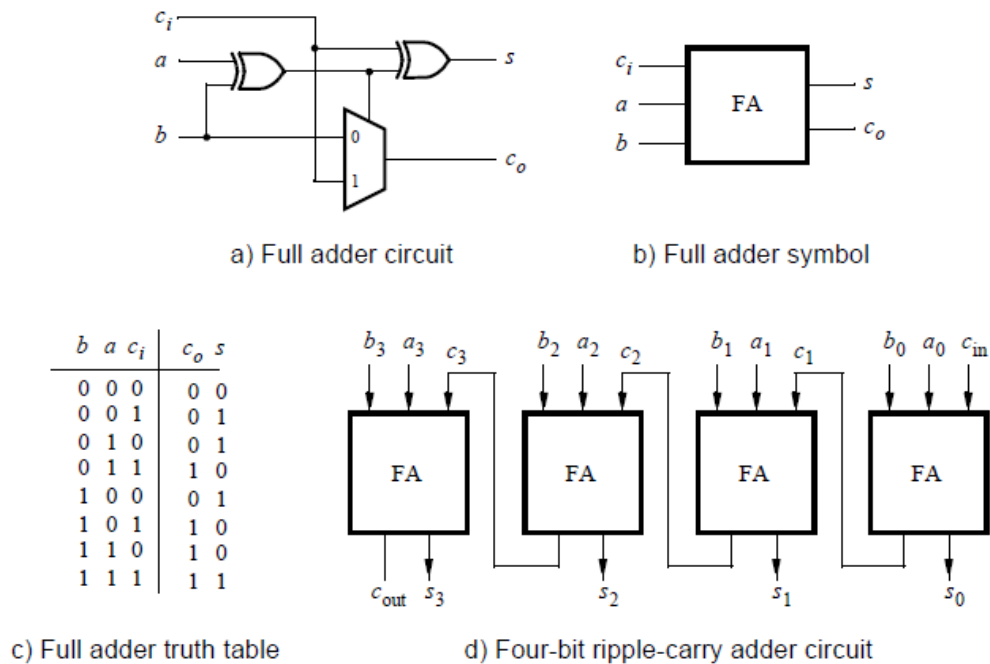


Figure 2: A ripple-carry adder circuit.

1. Create a new Quartus II project for the adder circuit. Write a Verilog module for the full adder subcircuit and write a top-level Verilog module that instantiates four instances of this full adder.
2. Use switches SW_{7-4} and SW_{3-0} to represent the inputs A and B , respectively. Use SW_8 for the carry-in c_{in} of the adder. Connect the SW switches to their corresponding red lights LEDR, and connect the outputs of the adder, c_{out} and S , to the green lights LEDG.
3. Include the necessary pin assignments for the DE2-series board, compile the circuit, and download it into the FPGA chip.
4. Test your circuit by trying different values for numbers A , B , and c_{in} .

Part IV 1-Digit BCD Adder

In part II we discussed the conversion of binary numbers into decimal digits. It is sometimes useful to build circuits that use this method of representing decimal numbers, in which each decimal digit is represented using four bits. This scheme is known as the *binary coded decimal* (BCD) representation. As an example, the decimal value 59 is encoded in BCD form as 0101 1001.

You are to design a circuit that adds two BCD digits. The inputs to the circuit are BCD numbers A and B , plus a carry-in, c_{in} . The output should be a two-digit BCD sum S_1S_0 . Note that the largest sum that needs to be handled by this circuit is $S_1S_0 = 9 + 9 + 1 = 19$. Perform the steps given below.

1. Create a new Quartus II project for your BCD adder. You should use the four-bit adder circuit from part III to produce a four-bit sum and carry-out for the operation $A + B$. A circuit that converts this five-bit result, which has the maximum value 19, into two BCD digits S_1S_0 can be designed in a very similar way as the binary-to-decimal converter from part II. Write your Verilog code using simple **assign** statements to specify the required logic functions—do not use other types of Verilog statements such as **if-else** or **case** statements for this part of the exercise.

2. Use switches SW_{7-4} and SW_{3-0} for the inputs A and B , respectively, and use SW_8 for the carry-in. Connect the SW switches to their corresponding red lights LEDR, and connect the four-bit sum and carry-out produced by the operation $A + B$ to the green lights LEDG. Display the BCD values of A and B on the 7-segment displays $HEX6$ and $HEX4$, and display the result S_1S_0 on $HEX1$ and $HEX0$.
3. Since your circuit handles only BCD digits, check for the cases when the input A or B is greater than nine. If this occurs, indicate an error by turning on the green light $LEDG_8$.
4. Include the necessary pin assignments for the DE2-series board, compile the circuit, and download it into the FPGA chip.
5. Test your circuit by trying different values for numbers A , B , and c_{in} .

Part V 2-Digit BCD Adder I

Design a circuit that can add two 2-digit BCD numbers, A_1A_0 and B_1B_0 to produce the three-digit BCD sum $S_2S_1S_0$. Use two instances of your circuit from part IV to build this two-digit BCD adder. Perform the steps below:

1. Use switches SW_{15-8} and SW_{7-0} to represent 2-digit BCD numbers A_1A_0 and B_1B_0 , respectively. The value of A_1A_0 should be displayed on the 7-segment displays $HEX7$ and $HEX6$, while B_1B_0 should be on $HEX5$ and $HEX4$. Display the BCD sum, $S_2S_1S_0$, on the 7-segment displays $HEX2$, $HEX1$ and $HEX0$.
2. Make the necessary pin assignments and compile the circuit.
3. Download the circuit into the FPGA chip, and test its operation.

Part VI 2-Digit BCD Adder II

In part V you created Verilog code for a two-digit BCD adder by using two instances of the Verilog code for a one-digit BCD adder from part IV. A different approach for describing the two-digit BCD adder in Verilog code is to specify an algorithm like the one represented by the following pseudo-code:

```

1   $T_0 = A_0 + B_0$ 
2  if ( $T_0 > 9$ ) then
3       $Z_0 = 10$ ;
4       $c_1 = 1$ ;
5  else
6       $Z_0 = 0$ ;
7       $c_1 = 0$ ;
8  end if
9   $S_0 = T_0 - Z_0$ 

10  $T_1 = A_1 + B_1 + c_1$ 
11 if ( $T_1 > 9$ )
then 12  $Z_1 = 10$ ;
13  $c_2 = 1$ ;
14 else
15  $Z_1 = 0$ ;
16  $c_2 = 0$ ;
17 end if
18  $S_1 = T_1 - Z_1$ 
19  $S_2 = c_2$ 

```

It is reasonably straightforward to see what circuit could be used to implement this pseudo-code. Lines 1, 9, 10, and 18 represent adders, lines 2-8 and 11-17 correspond to multiplexers, and testing for the conditions $T_0 > 9$ and $T_1 > 9$ requires comparators. You are to write Verilog code that corresponds to this pseudo-code. Note that you can perform addition operations in your Verilog code instead of the subtractions shown in lines 9 and 18. The intent of this part of the exercise is to examine the effects of relying more on the Verilog compiler to design the circuit by using **if-else** statements along with the Verilog $>$ and $+$ operators. Perform the following steps:

1. Create a new Quartus II project for your Verilog code. Use the same switches, lights, and displays as in part V. Compile your circuit.
2. Use the Quartus II RTL Viewer tool to examine the circuit produced by compiling your Verilog code. Compare the circuit to the one you designed in Part V.
3. Download your circuit onto the DE2-series board and test it by trying different values for numbers A_1A_0 and B_1B_0 .

Part VII 2-Digit Base-N Adder ($N=(\text{학번 끝자리})\%4+11$)

Design a circuit that can add two 2-digit base-N numbers, A_1A_0 and B_1B_0 to produce the three-digit base-N sum $S_2S_1S_0$. Use the same design approach as in part VI to build this two-digit base-N adder. Perform the steps below:

1. Use switches SW15-8 and SW7-0 to represent 2-digit base-N numbers A_1A_0 and B_1B_0 , respectively. The value of A_1A_0 should be displayed on the 7-segment displays HEX7 and HEX6, while B_1B_0 should be on HEX5 and HEX4. Display the base-N sum, $S_2S_1S_0$, on the 7-segment displays HEX3, HEX2 and HEX1.
2. Make the necessary pin assignments and compile the circuit
3. Download the circuit into the FPGA chip, and test its operation.